

Printable Assignment - Class: PHYS 2100 - Fall 2024 - Malikova Assignment: Chapter 21


Problem 1: As shown, three resistors are connected to a voltage source such that the resistors R_2 and R_3 are in parallel with one another, and that parallel combination is in series with resistor R_1 and the voltage source. Resistance values and the potential of the voltage source are as indicated in the figure.

Hossain, Phaner - phanerhossain2000@gmail.com

$$R_{eq} = 1 + \frac{1}{\frac{1}{13} + \frac{1}{6}} = 97/19 \Omega = 5.105 \Omega$$

$$I = \frac{V}{R_{eq}} = \frac{12}{5.105} = 2.35 \text{ A}$$

$$I_3 = \frac{9.65}{13}$$

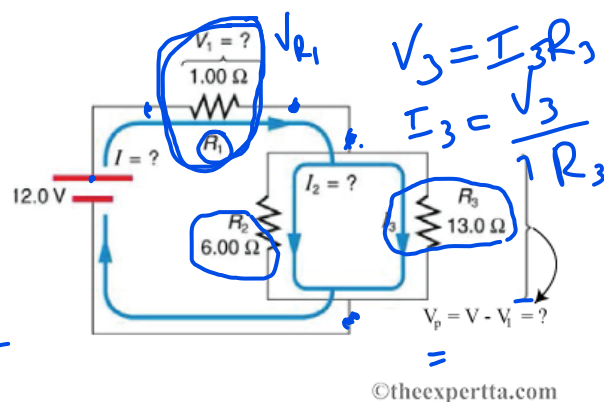

©theexpertta.com

@theexpertta.com - tracking id: 4N89-78-2D-49-A8AD-50799. In accordance with Expert TA's Terms of Service, copying this information to any solutions sharing website is strictly forbidden. Doing so may result in termination of your Expert TA Account.

Calculate the current, I_3 , in amperes, that passes through resistor R_3 .

Numeric : A numeric value is expected and not an expression.

$I_3 =$ _____ A

0.742 A


$$\frac{1}{\frac{1}{13} + \frac{1}{6}} = 4.105 \Omega$$

$$4.105 \times 2.35 = 9.647 \text{ V}$$

Problem 2: A circuit made up of 6 resistors is shown in the figure, with resistances $R_1 = 25 \Omega$, $R_2 = 65 \Omega$, $R_3 = 25 \Omega$, $R_4 = 65 \Omega$, $R_5 = 87 \Omega$, and $R_6 = 64 \Omega$. The total current going through the circuit is $I = 16 \text{ A}$.

Hossain, Phaner - phanerhossain2000@gmail.com

$$V = IR_{eq}$$

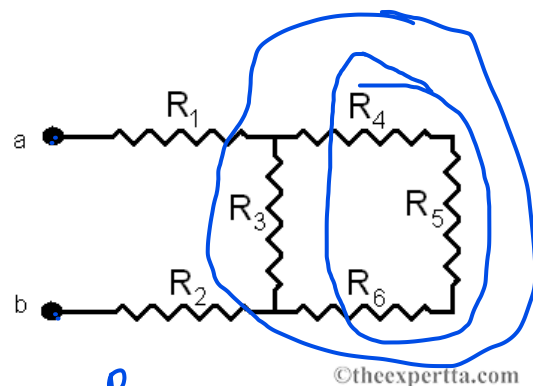

©theexpertta.com

@theexpertta.com - tracking id: 4N89-78-2D-49-A8AD-50799. In accordance with Expert TA's Terms of Service, copying this information to any solutions sharing website is strictly forbidden. Doing so may result in termination of your Expert TA Account.

Part (a) Express the equivalent resistance of the combination of R_4 , R_5 , and R_6 .

Expression :

$R_{eq} = R_4 + R_5 + R_6$

Select from the variables below to write your expression. Note that all variables may not be required.

$\alpha, \beta, \theta, d, g, I, m, R, R_1, R_2, R_3, R_4, R_5, R_6, t$

Part (b) Express the equivalent resistance of the combination of R_3 , R_4 , R_5 and R_6 .

Expression :

$R'_{eq} = \frac{1}{\frac{1}{R_3} + \frac{1}{R_4 + R_5 + R_6}}$

Select from the variables below to write your expression. Note that all variables may not be required.

$\alpha, \beta, \theta, d, g, I, m, R, R_1, R_2, R_3, R_4, R_5, R_6, t$

Part (c) Express the equivalent resistance R of the combination of R_1 , R_2 , R_3 , R_4 , R_5 and R_6 .

Expression :

$R = R_1 + R_2 + \frac{1}{\frac{1}{R_3} + \frac{1}{R_4 + R_5 + R_6}}$

Select from the variables below to write your expression. Note that all variables may not be required.

$\alpha, \beta, \theta, d, g, I, m, R, R_1, R_2, R_3, R_4, R_5, R_6, t$

Part (d) Calculate the numerical value of the equivalent resistance R in Ω .

Numeric : A numeric value is expected and not an expression.

$R =$ _____ /

Part (e) Express the potential difference between a and b, ΔV , in terms of the total current I and the equivalent resistance of the entire circuit R .

Expression :

$\Delta V =$ _____ $I R_{eq}$

Select from the variables below to write your expression. Note that all variables may not be required.

$\alpha, \beta, \theta, d, g, I, m, R, R_1, R_2, R_3, R_4, R_5, R_6, t$

Part (f) Calculate the numerical value of ΔV in V.


Numeric : A numeric value is expected and not an expression.

$\Delta V =$ _____ /

Problem 3: A circuit consisting of 5 resistors is shown in the graph. Their resistances are $R_1 = 19 \Omega$, $R_2 = 15 \Omega$, $R_3 = 89 \Omega$, $R_4 = 74 \Omega$, and $R_5 = 25 \Omega$, and the emf of the battery is $\varepsilon = 2.5 \text{ V}$. Suppose the internal resistance of the battery is zero.

Hossain, Phaner - phanerhossain2000@gmail.com

$$\varepsilon = I R_{eq}$$

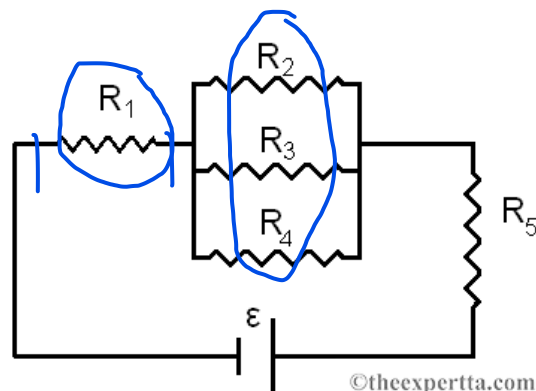

@theexpertta.com - tracking id: 4N89-78-2D-49-A8AD-50799. In accordance with Expert TA's Terms of Service, copying this information to any solutions sharing website is strictly forbidden. Doing so may result in termination of your Expert TA Account.

Part (a) Express the equivalent resistance of the combination of R_2 , R_3 , and R_4 .

Expression :

$R_{eq} =$ _____

$$1 / \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right)$$

Select from the variables below to write your expression. Note that all variables may not be required.

R_2, R_3, R_4

Part (b) Express the total resistance of the circuit R in terms of R_1 , R_2 , R_3 , R_4 , and R_5 .

Expression :

$R =$ _____ $R_1 + R_5 + 1 / \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right)$

Select from the variables below to write your expression. Note that all variables may not be required.

R_1, R_2, R_3, R_4, R_5

Part (c) Calculate the numerical value of the total resistance R in ohms.

Numeric : A numeric value is expected and not an expression.

$R =$ _____ Ω

Part (d) Express the current I through R_1 in terms of the emf ε and the equivalent resistance R .

Expression :

$I =$ _____

Select from the variables below to write your expression. Note that all variables may not be required.

ε, R

Part (e) Calculate the numerical value of I in amps.

Numeric : A numeric value is expected and not an expression.

$I =$ _____ A

$$P = IV = \frac{\varepsilon^2}{R} = I^2 R$$

Part (f) Express the power P dissipated by R_1 using I and R_1 .

Expression :

$$P = I^2 R_1$$

Select from the variables below to write your expression. Note that all variables may not be required.

I, R_1

Part (g) Calculate the numerical value of the power dissipated by R_1, P , in watts.


Numeric : A numeric value is expected and not an expression.

$$P = \text{_____} \text{ W}$$

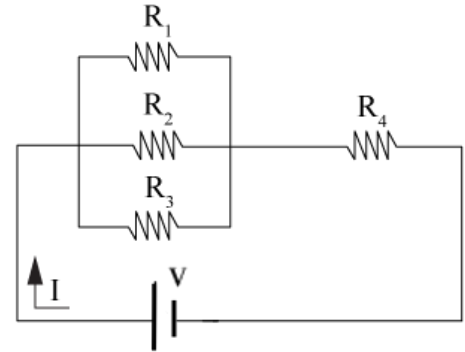Problem 4: Consider the circuit in the following diagram, where the resistances are $R_1 = 0.35R$, $R_2 = 3R$, $R_3 = 0.55R$, and $R_4 = 3R$, where $R = 19 \Omega$. The circuit is connected to a $V = 2.7 \text{ V}$ source.

Hossain, Phaner - phanerhossain2000@gmail.com

$$R_4 + \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$



$$P = \frac{V^2}{R_{eq}}$$

©theexpertta.com

@theexpertta.com - tracking id: 4N89-78-2D-49-A8AD-50799. In accordance with Expert TA's Terms of Service, copying this information to any solutions sharing website is strictly forbidden. Doing so may result in termination of your Expert TA Account.

Part (a) Input an expression for the equivalent resistance of the circuit in terms of R_1, R_2, R_3 , and R_4 .

Expression :

$$R_{eq} = \text{_____}$$

Select from the variables below to write your expression. Note that all variables may not be required.

$\alpha, \beta, \theta, a, b, d, g, h, j, k, m, P, R_1, R_2, R_3, R_4, R_{eq}, S, t, V$

Part (b) Input an expression using the R_{eq} and V for power expended by the circuit.

Expression :

$$P = \frac{V^2}{R_{eq}}$$

Select from the variables below to write your expression. Note that all variables may not be required.

$\alpha, \beta, \theta, d, g, h, m, P, R_1, R_2, R_3, R_4, R_{eq}, t, V$

Part (c) What is the power P , in watts?

Numeric : A numeric value is expected and not an expression.

$$P = \text{_____}$$

Problem 5: A current of $I = 4.9 \text{ A}$ passes through the circuit shown, where $R = 39 \Omega$.


Hossain, Phaner - phanerhossain2000@gmail.com

$$\frac{1}{\frac{1}{6} + \frac{1}{2} + \frac{1}{7}} = 1.2353R$$

$$\frac{1}{\frac{1}{12353} + \frac{1}{15}} = 1.141R$$

$$\frac{1}{\frac{1}{2} + \frac{1}{9.141}} = 1.641R$$

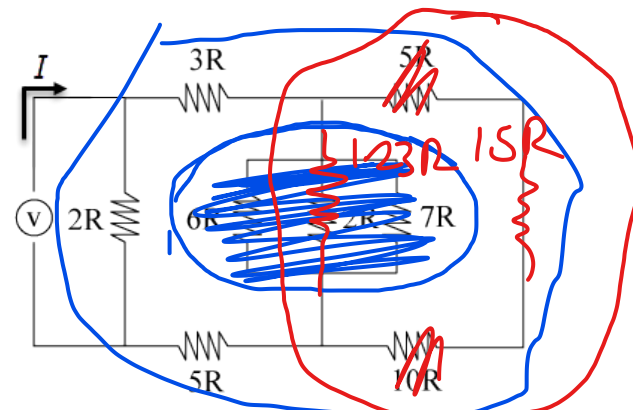@theexpertta.com - tracking id: 4N89-78-2D-49-A8AD-50799. In accordance with Expert TA's Terms of Service, copying this information to any solutions sharing website is strictly forbidden. Doing so may result in termination of your Expert TA Account.



©theexpertta.com

$$1.141R + 3R + 5R$$

$$9.141R$$

in termination of your Expert TA Account.

Part (a) In terms of R , I , and numeric values, write an expression for the voltage of the source, V .

Expression :

$$V = 1.64 I R$$

Select from the variables below to write your expression. Note that all variables may not be required.

$\alpha, \beta, \theta, a, d, g, h, I, j, k, m, P, R, S, t$

Part (b) What is the voltage, V in volts?

Numeric : A numeric value is expected and not an expression.

$$V =$$

Problem 6: Consider the circuit in the diagram, with sources of emf listed below.

Randomized Variables

$$\mathcal{E}_1 = 28 \text{ V}$$

$$\mathcal{E}_2 = 42 \text{ V}$$

$$\mathcal{E}_3 = 8.5 \text{ V}$$

$$\mathcal{E}_4 = 33 \text{ V}$$

Hossain, Phaner - phanerhossain2000@gmail.com

KCL

$$I_3 = I_1 + I_2 \quad \text{--- (1)}$$

KVL for (1)

$$\mathcal{E}_2 - I_2 r_2 - I_2 R_2 + I R_3 + I_1 r_1 - \mathcal{E}_1 + R_1 I_1 = 0$$

$$42 - 40.5 I_2 + 25.1 I_1 - 28 = 0$$

@theexpertta.com - tracking id: 4N89-78-2D-49-A8AD-50799. In accordance with Expert TA's Terms of Service, copying this information to any solutions sharing website is strictly forbidden. Doing so may result in termination of your Expert TA Account.

Part (a) Find I_1 in amps.

Numeric : A numeric value is expected and not an expression.

$$I_1 = -0.115 \text{ A}$$

Part (b) Find I_2 in amps.

Numeric : A numeric value is expected and not an expression.

$$I_2 = 0.2496$$

Part (c) Find I_3 in amps.

Numeric : A numeric value is expected and not an expression.

$$I_3 = 0.0945$$


Problem 7: Consider a circuit shown in the figure. Ignore the internal resistances of the batteries.

Hossain, Phaner - phanerhossain2000@gmail.com

$$-I_3 R_3 + \mathcal{E}_1 - R_1 I_1 = 0 \quad \checkmark$$

$$I_3 + I_2 = I_1 \quad \checkmark$$
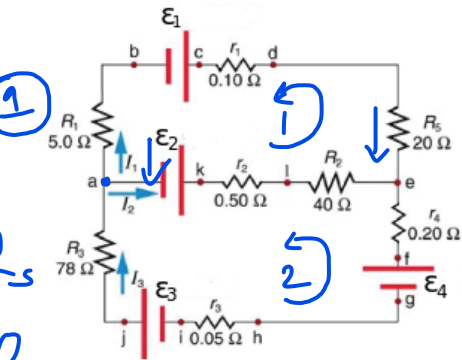
$$R_1 I_1 - \mathcal{E}_1 - \mathcal{E}_2 + I_2 R_2 = 0$$





©theexpertta.com

$$25.1 I_1 - 40.5 I_2 = -14 \quad \text{--- (2)}$$

$$I_3 R_3 - \mathcal{E}_3 + I_3 r_3 + \mathcal{E}_4 + r_4 I_3 + R_2 I_2 + I_2 r_2 - \mathcal{E}_2 = 0$$
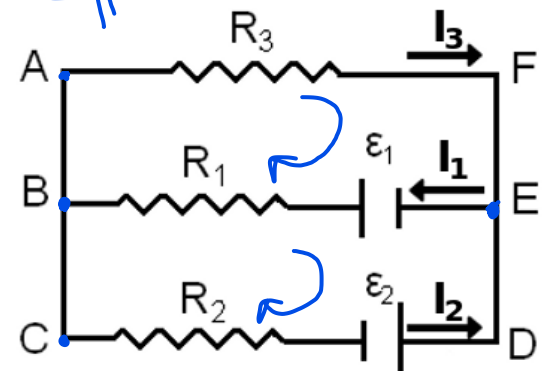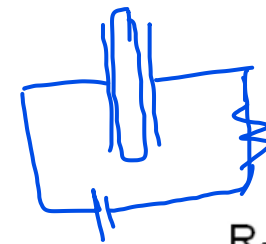
$$78.25 I_3 + 40.5 I_2 = 17.5 \quad \text{--- (3)}$$



©theexpertta.com

@theexpertta.com - tracking id: 4N89-78-2D-49-A8AD-50799. In accordance with Expert TA's Terms of Service, copying this information to any solutions sharing website is strictly forbidden. Doing so may result in termination of your Expert TA Account.

Part (a) Express the current I_1 going through resistor R_1 in terms of the currents I_2 and I_3 going through resistors R_2 and R_3 . Use the direction of the currents as specified in the figure.

Expression :

$$I_1 = I_2 + I_3$$

Select from the variables below to write your expression. Note that all variables may not be required.

$\mathcal{E}_1, \mathcal{E}_2, \alpha, \beta, \theta, d, g, I_1, I_2, I_3, m, R_1, R_2, R_3, t$

Part (b) Write the equation of potential change in loop EBAF in terms of the circuit elements.

Expression :

$$\Sigma V_{\text{EBAF}} = -I_3 R_3 + \mathcal{E}_1 - I_1 R_1$$

Select from the variables below to write your expression. Note that all variables may not be required.

$\mathcal{E}_1, \mathcal{E}_2, \alpha, \beta, \theta, d, g, I_1, I_2, I_3, m, R_1, R_2, R_3, t$

Part (c) Write the equation of potential change in loop DCAF in terms of the circuit elements.

Expression :

$$\Sigma V_{\text{DCAF}} = I_1 R_1 - \mathcal{E}_1 - \mathcal{E}_2 + I_3 R_3$$

Select from the variables below to write your expression. Note that all variables may not be required.

$\mathcal{E}_1, \mathcal{E}_2, \alpha, \beta, \theta, d, g, I_1, I_2, I_3, m, R_1, R_2, R_3, t$

Part (d) Solve the three equations to get I_3 .

Expression :

$$I_3 = \frac{\mathcal{E}_2}{2R_3}$$

Select from the variables below to write your expression. Note that all variables may not be required.

$\mathcal{E}_1, \mathcal{E}_2, \alpha, \beta, \theta, d, g, I_1, I_2, I_3, m, R_1, R_2, R_3, t$

Part (e) Now let $\mathcal{E}_1 = 34 \text{ V}$, $\mathcal{E}_2 = 16 \text{ V}$, $R_1 = 1 \Omega$, $R_2 = 1 \Omega$, and $R_3 = 2 \Omega$. Calculate the numerical value of I_3 in amps.

Numeric : A numeric value is expected and not an expression.

$$I_3 = \text{A}$$

Part (f) Calculate the numerical value of I_2 in amps.

Numeric : A numeric value is expected and not an expression.

$$I_2 = \text{A}$$

Part (g) Calculate the numerical value of I_1 in amps.

Numeric : A numeric value is expected and not an expression.

$$I_1 = \text{A}$$

Problem 8: Two capacitors of capacitance $3C$ and $5C$ (where $C = 0.055 \text{ F}$) are connected in series with a resistor of resistance $R = 5.5 \Omega$.


Randomized Variables

$$R = 5.5 \Omega$$

$$C = 0.055 \text{ F}$$

Hossain, Phaner - phanerhossain2000@gmail.com
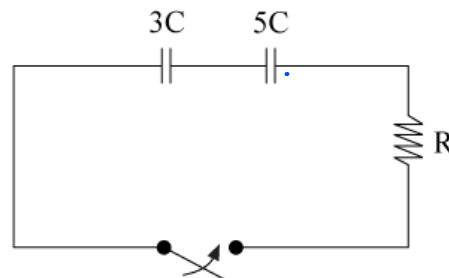
$$\frac{1}{\frac{1}{3} + \frac{1}{5}} = \frac{15}{8} \times 0.055$$



©theexpertta.com

@theexpertta.com - tracking id: 4N89-78-2D-49-A8AD-50799. In accordance with Expert TA's Terms of Service, copying this information to any solutions sharing website is strictly forbidden. Doing so may result in termination of your Expert TA Account.

Part (a) How long will it take the amount of charge in the circuit to drop by 75% in seconds?

Numeric : A numeric value is expected and not an expression.

$$t = \text{s}$$

Part (b) If the circuit was charged by a 10.0 V source how much total charge (in C) did both capacitors have in them to begin with?

$$Q = CV$$

$$Q_0 = \frac{15}{8} \times 0.055 \times 10$$


Numeric : A numeric value is expected and not an expression.

$$q_i = \underline{\hspace{2cm}} \text{ C}$$

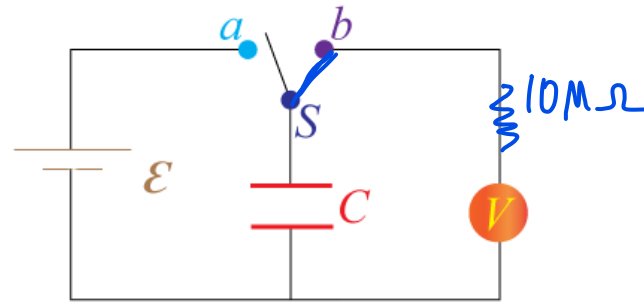Problem 9: While preparing a laboratory experiment on capacitors, you connect an $\varepsilon = 7.5 \text{ V}$ DC power supply to fully charge an old capacitor that is marked $C = 220 \mu\text{F}$. Your lab assistant hooks up the circuit as shown below. When the switch S is at point a , the capacitor is connected to the power supply. When the switch S is at point b , the capacitor is disconnected from the power supply and connected to a voltmeter, V . The voltmeter has an internal resistance $R = 10.0 \text{ M}\Omega$.

Hossain, Phaner - phanerhossain2000@gmail.com

$$Q_0 = C\varepsilon = 7.5 \times 220 \times 10^{-6} = 1.65 \text{ mC}$$



©theexpertta.com

@theexpertta.com - tracking id: 4N89-78-2D-49-A8AD-50799. In accordance with Expert TA's Terms of Service, copying this information to any solutions sharing website is strictly forbidden. Doing so may result in termination of your Expert TA Account.

Part (a) The capacitor is initially uncharged, when the switch is moved to position a , hooking the capacitor C to the power supply. What will happen to the charge on the capacitor?

MultipleChoice :

- 1) It will remain unchanged.
- 2) It will very slowly increase until the capacitor is disconnected from the power supply.
- ☒ 3) It will quickly (but not instantaneously) increase to a maximum value.
- 4) It will quickly (but not instantaneously) increase until the capacitor is disconnected from the power supply.
- 5) It will instantaneously increase to a maximum value
- 6) It will very slowly increase, eventually reaching a maximum value.

$$10^1 \times 10^6 = 10^7$$

Part (b) Calculate the charge on the capacitor (in Coulombs) when it is fully charged by the power supply.

Numeric : A numeric value is expected and not an expression.

$$q = \underline{1.65 \times 10^{-3} \text{ C}}$$

$$\ln(2) / 10^7 \times 220 \times 10^{-6}$$

Part (c) After the capacitor is fully charged, you switch the switch to position b at time $t = 0$ seconds. The voltmeter initially reads 7.5 V . After how much elapsed time (in seconds) would you expect the voltmeter to read $1/2$ its initial value?

Numeric : A numeric value is expected and not an expression.

$$t_{1/2} = \underline{3.15 \times 10^{-4} \text{ s}}$$

$$C = \frac{KA\varepsilon_0}{d}$$

Part (d) When you actually move the switch to point b , the voltmeter shows it only takes 1000.0 s for the voltage to drop to half its initial value. Which of the following are possible explanations of the observed behavior of this circuit? Select all that apply.

MultipleSelect :

- ☒ 1) The dielectric in the capacitor has degraded over time, decreasing the effective capacitance of the capacitor.
- 2) The capacitor has been physically damaged, effectively bringing the plates closer together. ☒
- ☒ 3) The internal resistance of the voltmeter is significantly lower than $10 \text{ M}\Omega$.
- 4) The internal resistance of the power supply is acting in series with the capacitor, decreasing the overall resistance of the circuit.
- ☒ 5) The internal resistance of the power supply is acting in parallel with the capacitor, decreasing the overall resistance of the circuit.

$$\begin{array}{c} 2 \quad 2 \\ \text{---} \text{---} \end{array} = 4 \quad \begin{array}{c} 3 \quad 4 \quad 50 \\ \text{---} \text{---} \text{---} \end{array}$$


$R_{eq} > 50$

$$\begin{array}{c} 2 \\ \text{---} \text{---} \end{array} = 1 \Omega \quad \begin{array}{c} 1 \\ 50 \\ 4 \\ 3 \end{array}$$

$R_{eq} < 1$

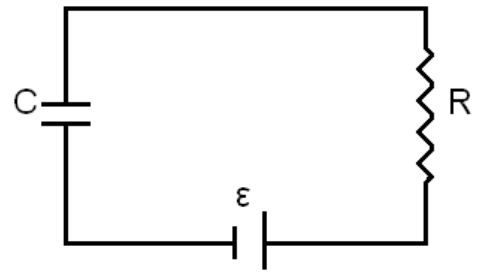Problem 10: An uncharged capacitor with $C = 9 \mu\text{F}$ and a resistor with $R = 95 \Omega$ are connected in series with a battery of $\epsilon = 2.5 \text{ V}$.

Hossain, Phaner - phanerhossain2000@gmail.com



©theexpertta.com

CE

@theexpertta.com - tracking id: 4N89-78-2D-49-A8AD-50799. In accordance with Expert TA's Terms of Service, copying this information to any solutions sharing website is strictly forbidden. Doing so may result in termination of your Expert TA Account.

Part (a) Express the time constant τ in terms of R and C .

Expression :

$\tau = RC$

Select from the variables below to write your expression. Note that all variables may not be required.

$\alpha, \beta, \epsilon, \theta, C, d, g, h, i, j, k, m, P, R, t$

Part (b) Calculate the numerical value of τ in microseconds.

Numeric : A numeric value is expected and not an expression.

$\tau = \frac{1}{1} \mu\text{s}$

Part (c) Express the maximum charge Q on the capacitor in terms of C and ϵ .

Expression :

$Q = CE$

Select from the variables below to write your expression. Note that all variables may not be required.

$\alpha, \beta, \epsilon, \theta, C, d, g, h, i, j, k, m, P, R, t$

Part (d) Calculate the numerical value of Q in microcoulombs.

Numeric : A numeric value is expected and not an expression.

$Q = \frac{1}{1} \mu\text{C}$